

COAL Lab # 01

Verilog (HDL) Programming Fundamentals

Name: Saad Nisar Butt

Reg. no: cs211246

Class: BS-CS 3C-1

Lab Exercises:

Combinational Circuits:

Literature Review:

Combinational circuits are made up of basic logic gates such as and, or and not gates. A combinational circuit consists of logic gates whose outputs at any time are determined from only the present combination of inputs. Their operations are determined by a set of Boolean functions. Outputs of the combinational logic circuits depend only on the present inputs. Here, we have three inputs, two are XORed and that two are ANDed and both outputs with another input are ORed to perform certain logic.


Task 01:

Implement combinational logic circuit using Verilog HDL.

Truth Table:

A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Block Diagram:

 

Boolean Equation:

$$X = A \oplus B + A \cdot B + C$$

Verilog Code:

design.v

```
module combinational_circuit(A, B, C, Q);

    //inputs
    input A, B, C;
    output Q;

    //interim signals
    wire A_xor_B;
    wire A_and_B;

    //logic designing
    assign A_xor_B = A ^ B;
    assign A_and_B = A & B;
    // final output
    assign Q = C | A_xor_B | A_and_B;

endmodule

// assign Q = (A ^ B) | (A & B) | C
```

testbench.v

```
module tb();

    reg A, B, C;
    wire Q;

    // module declaration
    combinational_circuit dut (
        .A(A), .B(B), .C(C), .Q(Q)
    );

    initial begin
```

```
A <= 1'b0;
B <= 1'b0;
C <= 1'b0;
#100;

A <= 1'b0;
B <= 1'b0;
C <= 1'b1;
#100;

A <= 1'b0;
B <= 1'b1;
C <= 1'b0;
#100;

A <= 1'b0;
B <= 1'b1;
C <= 1'b1;
#100;


A <= 1'b1;
B <= 1'b0;
C <= 1'b0;
#100;

A <= 1'b1;
B <= 1'b0;
C <= 1'b1;
#100;
A <= 1'b1;
B <= 1'b1;
C <= 1'b0;
#100;
A <= 1'b1;
B <= 1'b1;
C <= 1'b1;
#100;
end

initial begin
    $dumpfile("dump.vcd");
    $dumpvars(0);
end
```

```
endmodule
```

Waveforms:

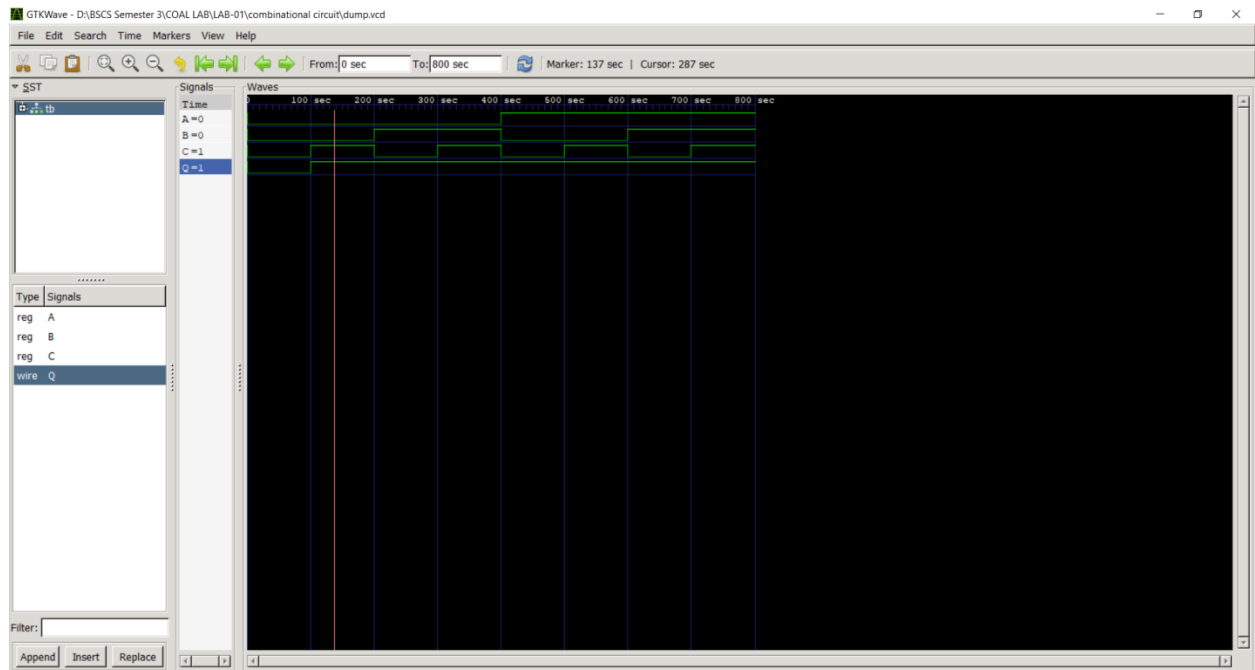

Task 02:

Implement sequential logic circuit using Verilog HDL.


Literature Review:

Sequential Circuits have memory elements in addition to logic gates. They possess the ability to store the output for the computation of logic. Their outputs are a function of the inputs and the state of the storage elements. They depend upon current inputs as well as past inputs. They also include a time sequence of inputs and internal states. In this task, a combinational circuit is designed as a sequential circuit in which the output is stored in a flop just to show an example of sequential circuits.

Truth Table:

A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Block Diagram:

 

Verilog Code:

design.v

```
module sequential_circuit(A, B, C, clk, reset, Q);

    // inputs
    input A, B, C, clk, reset;
    // output
    output Q;

    //interim signals
    wire A_xor_B;
    wire A_and_B;
    wire A_or_B_C;
    reg flop;

    //logic designing
    assign A_xor_B = A ^ B;
    assign A_and_B = A & B;
    assign A_or_B_C = C | A_xor_B | A_and_B;

    always @(posedge clk) begin
        if(reset == 1'b1)
```

```

        begin
            flop <= 1'b0;
        end
        else begin
            flop <= A_or_B_C;
        end
    end

    assign Q = flop;

endmodule

// assign Q = (A ^ B) | (A & B) | C

```

testbench.v

```

module tb();

    reg A, B, C, clk, reset;
    wire Q;

    // module declaration
    sequential_circuit dut (
        .A(A), .B(B), .C(C), .clk(clk), .reset(reset), .Q(Q)
    );

    always begin
        clk <= 1'b0;
        #50;
        clk <= 1'b1;
        #50;
    end

    initial begin
        reset <= 1'b1;
        #100;
        reset <= 1'b0;

        A <= 1'b0;
        B <= 1'b0;
        C <= 1'b0;
        #100;
    end
endmodule

```



```
A <= 1'b0;
B <= 1'b0;
C <= 1'b1;
#100;

A <= 1'b0;
B <= 1'b1;
C <= 1'b0;
#100;
A <= 1'b0;
B <= 1'b1;
C <= 1'b1;
#100;

A <= 1'b1;
B <= 1'b0;
C <= 1'b0;
#100;


A <= 1'b1;
B <= 1'b0;
C <= 1'b1;
#100;
A <= 1'b1;
B <= 1'b1;
C <= 1'b0;
#100;

A <= 1'b1;
B <= 1'b1;
C <= 1'b1;
#100;
$finish;
end

initial begin
    $dumpfile("dump.vcd");
    $dumpvars(0);
end

endmodule
```

Waveforms:

 

In Lab Tasks:

Task 03:


Create a Verilog module for half adder. Make a test bench for all the possible input combinations and attach the waveforms.

Half Adder

Literature Review:

Half adder is a combinational and arithmetic logic circuit which is used to add two binary digits. The adder accepts two inputs and produces two outputs, one is sum and a carry out. Inputs are XORed to produce sum and then ANDed to produce carry out. If two half adders are cascaded, one full adder can be formed which can compute more than two bits addition.

Block Diagram:

 

Truth Table:

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	1	1

Boolean Equation:

$$S = A \oplus B$$

$$C = A \cdot B$$

Verilog Code:

design.v

```
module half_adder(A, B, S, Cout);  
  
    // inputs  
    input A, B, C;  
    // outputs  
    output S, Cout;  
  
    //logic designing  
    assign S = A ^ B;  
    assign Cout = A & B;  
  
endmodule
```

testbench.v

```
module tb();  
  
    reg A, B;  
    wire S, Cout;
```

```
// module declaration
half_adder dut (
    .A(A), .B(B), .S(S), .Cout(Cout)
);

initial begin
    A <= 1'b0;
    B <= 1'b0;
    #100;

    A <= 1'b1;
    B <= 1'b0;
    #100;

    A <= 1'b0;
    B <= 1'b1;
    #100;


    A <= 1'b1;
    B <= 1'b1;
    #100;

end

initial begin
    $dumpfile("dump.vcd");
    $dumpvars(0);
end

endmodule
```

Waveforms:

 

Task 04:

Create a two bit counter. Make a test bench for all the possible input combinations and attach the waveforms.

Sequential Circuit:


Literature Review:

Sequential circuits have certain applications, one of them is 2-bit counter. Counter simply increments one in the previous value and store it for the next computation. On every clock cycle, under defined conditions, one will add in the input and it will be stored in memory element and then for next cycle it will repeat the process until it reaches the limit of bits storage. And if the delay will still be there the cycle will restart from zero and keep on incrementing one.

Truth Table:

CLK	Q1	Q2
Initial	0	0
1	0	1
2	1	0
3	1	1
4	0	0

Block Diagram:

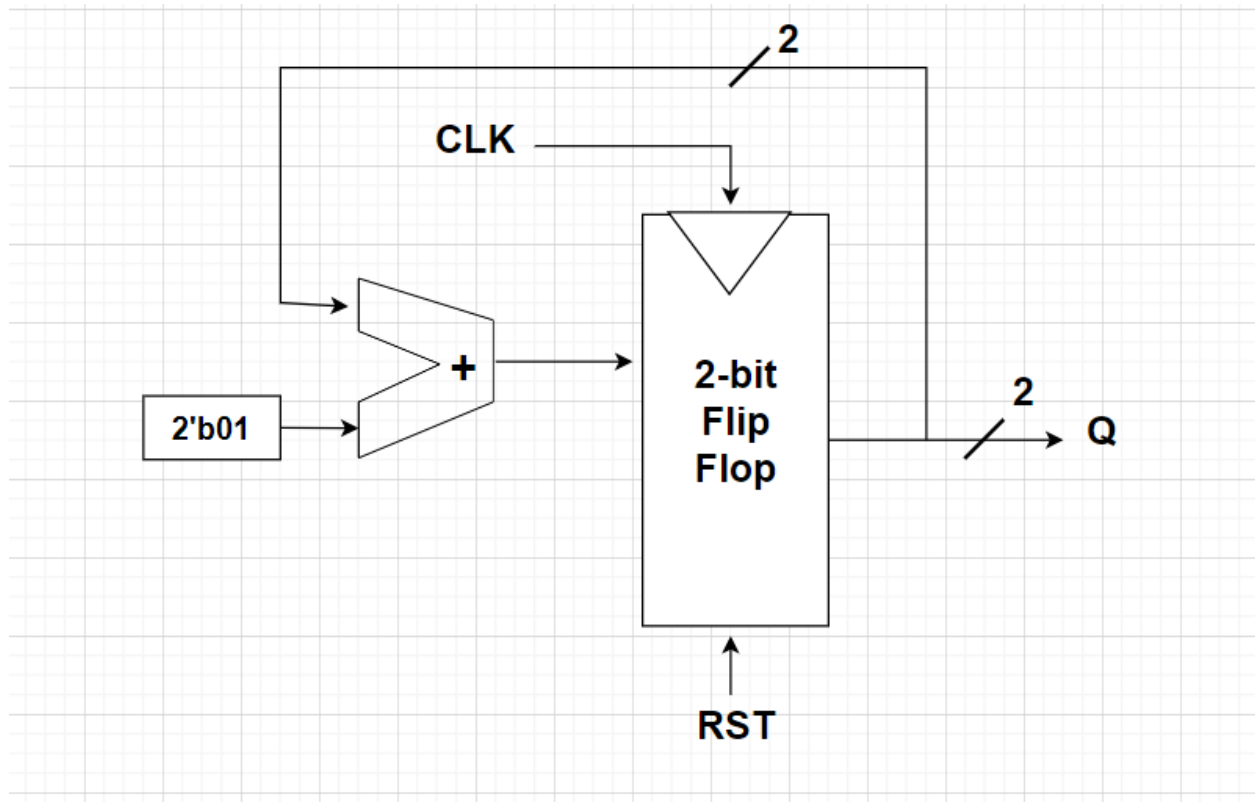

Verilog Code:

design.v

```
module two_bit_counter(input clk, reset, output[1:0] Q);  
  
    //input  
    reg[1:0] flop;  
  
    always @(posedge clk) begin  
        if(reset == 1'b1)  
            begin  
                flop <= 2'b00;  
            end  
        else begin  
            flop <= flop + 2'b01;  
        end  
    end  
end
```



```
    assign Q = flop;

endmodule
```

testbench.v

```
module tb();

    reg clk, reset;
    wire[1:0] Q;

    // module declaration
    two_bit_counter dut (
        .clk(clk), .reset(reset), .Q(Q)
    );

    // clock cycle
    always begin
        clk <= 1'b0;
        #50;
        clk <= 1'b1;
        #50;
    end


    initial begin
        reset <= 1'b1;
        #100;
        reset <= 1'b0;
        #500;

        $finish;
    end

    initial begin
        $dumpfile("dump.vcd");
        $dumpvars(0);
    end

endmodule
```

Waveforms:

 

Post Lab Task:


Task 05:

Below is the gate level circuit for the combinational circuit. Write down a data flow model for it. Hint: First write the Boolean expression for the below circuit.

Literature Review:

Combinational circuits are made up of basic logic gates such as and, or and not gates. A combinational circuit consists of logic gates whose outputs at any time are determined from only the present combination of inputs. Their operations are determined by set of Boolean functions. Mainly, combinational circuits are used to design complex logics such as alarm system for stuck elevator or traffic lights etc. Here, we have four inputs, A,B,C and D. which are computed logically using AND, OR, NOT and XOR gate performing certain logic.

Block Diagram:

 

Truth Table:

A	B	C	D	Z
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

Boolean Equation:

$$Z = A + \overline{(C + D)} \oplus (B \oplus D) + B.C$$

Verilog Code:

design.v

```
module combinational_circuit(A, B, C, D, Z);  
    // inputs  
    input A, B, C, D;  
  
    // interim wires  
    wire B_xor_D;  
    wire B_and_C;  
    wire C_or_D;
```

```

wire not_C_or_D;
wire A_or_not_C_or_D;
wire B_xor_D_or_B_and_C;

// output
output Z;

// assignment with logical operations
assign B_xor_D = B ^ D;
assign B_and_C = B & C;
assign C_or_D = C | D;
assign not_C_or_D = !(C_or_D);
assign A_or_not_C_or_D = A | not_C_or_D;
assign B_xor_D_or_B_and_C = B_xor_D | B_and_C;
// final output
assign Z = A_or_not_C_or_D ^ B_xor_D_or_B_and_C;

endmodule

// assign Z = (A | (!(C | D))) ^ ((B ^ D) | (B & C));

```

testbench.v

```

module tb();
    reg A, B, C, D;
    wire Z;

    // module declaration
    combinational_circuit dut (
        .A(A), .B(B), .C(C), .D(D), .Z(Z)
    );

    initial begin
        A <= 1'b0;
        B <= 1'b0;
        C <= 1'b0;
        D <= 1'b0;
        #100;

        A <= 1'b0;
        B <= 1'b0;
        C <= 1'b0;
        D <= 1'b1;
        #100;
    end

```

```
A <= 1'b0;  
B <= 1'b0;  
C <= 1'b1;  
D <= 1'b0;  
#100;
```

```
A <= 1'b0;  
B <= 1'b0;  
C <= 1'b1;  
D <= 1'b1;  
#100;
```

```
A <= 1'b0;  
B <= 1'b1;  
C <= 1'b0;  
D <= 1'b0;  
#100;
```

```
A <= 1'b0;  
B <= 1'b1;  
C <= 1'b0;  
D <= 1'b1;  
#100;
```

```
A <= 1'b0;  
B <= 1'b1;  
C <= 1'b1;  
D <= 1'b0;  
#100;  
A <= 1'b0;  
B <= 1'b1;  
C <= 1'b1;  
D <= 1'b1;  
#100;
```

```
A <= 1'b1;  
B <= 1'b0;  
C <= 1'b0;  
D <= 1'b0;  
#100;
```

```
A <= 1'b1;  
B <= 1'b0;  
C <= 1'b0;
```

```
D <= 1'b1;
#100;

A <= 1'b1;
B <= 1'b0;
C <= 1'b1;
D <= 1'b0;
#100;
A <= 1'b1;
B <= 1'b0;
C <= 1'b1;
D <= 1'b1;
#100;

A <= 1'b1;
B <= 1'b1;
C <= 1'b0;
D <= 1'b0;
#100;

A <= 1'b1;
B <= 1'b1;
C <= 1'b0;
D <= 1'b1;
#100;

A <= 1'b1;
B <= 1'b1;
C <= 1'b1;
D <= 1'b0;
#100;


A <= 1'b1;
B <= 1'b1;
C <= 1'b1;
D <= 1'b1;
#100;

end

initial begin
    $dumpfile("dump.vcd");
    $dumpvars(0);
end
```

```
endmodule
```

Waveform:

 

* ----- *